

Passive π Filter Analysis

Author Rodrigo

Analysis

Select a value for L in the π filter showed in figure 1 so that $V_o = \frac{1}{10} V_{in}$ at $f = 100$ Hz. Select $C = 10 \mu\text{F}$

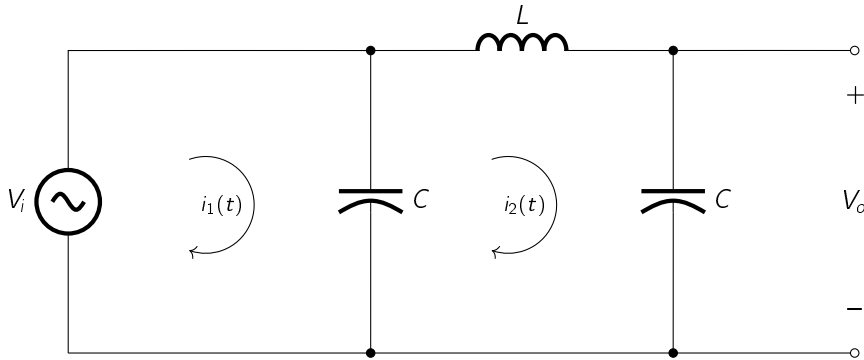


Figure 1: passive π filter

Solution

In this example, we find the transfers function by first transforming the circuit into the s domain

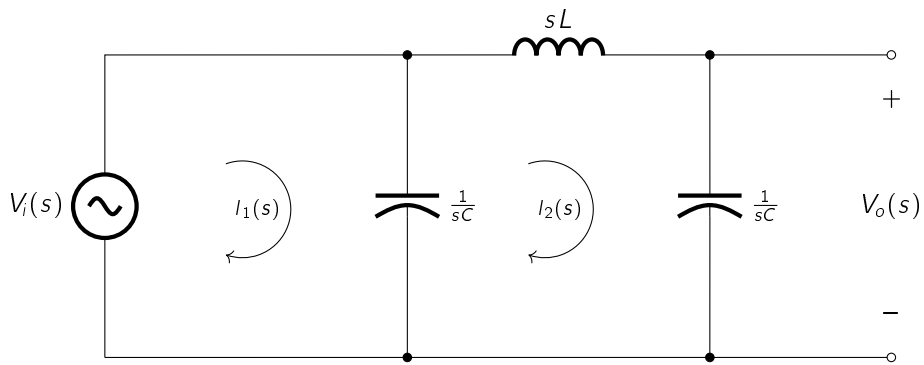


Figure 2: passive π filter

By KVL (Kirchhoff Voltage Law), the sum of voltage transforms around the loop is

$$\begin{aligned}
 V_i(s) - \frac{1}{sC}(I_1(s) - I_2(s)) &= 0 \\
 V_i(s) - \frac{1}{sC}I_1(s) + \frac{1}{sC}I_2(s) &= 0 \\
 \frac{1}{sC}I_1(s) - \frac{1}{sC}I_2(s) &= V_i(s)
 \end{aligned} \tag{1}$$

the same step for loop 2 gives

$$\begin{aligned}
-\frac{1}{sC} [I_2(s) - I_1(s)] - sL I_2(s) - \frac{1}{sC} I_2(s) &= 0 \\
-\frac{1}{sC} I_2(s) + \frac{1}{sC} I_1(s) - sL I_2(s) - \frac{1}{sC} I_2(s) &= 0 \\
\frac{1}{sC} I_1(s) - \left[sL + \frac{1}{sC} + \frac{1}{sC} \right] I_2(s) &= 0 \\
\frac{1}{sC} I_1(s) - \left[sL + \frac{2}{sC} \right] I_2(s) &= 0
\end{aligned} \tag{2}$$

From (1) and (2)

$$v_o = \begin{cases} \frac{1}{sC} I_1(s) - \frac{1}{sC} I_2(s) = V_i(s) \\ \frac{1}{sC} I_1(s) - \left[sL + \frac{2}{sC} \right] I_2(s) = 0 \end{cases} \tag{3}$$

We have a 2x2 linear system, solving for $I_1(s)$ in 3(b) we get

$$\begin{aligned}
\frac{1}{sC} I_1(s) &= \left[sL + \frac{2}{sC} \right] I_2(s) \\
I_1(s) &= sC \left[sL + \frac{2}{sC} \right] I_2(s) \\
I_1(s) &= (s^2 CL + 2) I_2(s)
\end{aligned} \tag{4}$$

Replacing (4) in (3a) yields

$$\begin{aligned}
\frac{1}{sC} [s^2 CL + 2] I_2(s) - \frac{1}{sC} I_2(s) &= V_i(s) \\
\left[sL + \frac{2}{sC} \right] I_2(s) - \frac{1}{sC} I_2(s) &= V_i(s) \\
\left[\frac{s^2 LC + 2}{sC} \right] I_2(s) - \frac{1}{sC} I_2(s) &= V_i(s) \\
\left[\frac{s^2 LC + 2 - 1}{sC} \right] I_2(s) &= V_i(s) \\
I_2(s) &= \frac{sC}{1 + s^2 LC} V_i(s)
\end{aligned} \tag{5}$$

Now, the output voltage is

$$V_o(s) = \frac{1}{sC} I_2(s) \tag{6}$$

Replacing (5) in (6) yields

$$V_o(s) = \frac{1}{sC} \left[\frac{sC}{1 + s^2 LC} \right] V_i(s) = \left[\frac{1}{1 + s^2 LC} \right] \tag{7}$$

The transfer function is

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{1}{1 + s^2 LC} \tag{8}$$

The frequency response is obtained by substituting $s = j\omega$ into $H(s)$

$$H(\omega) = H(s) \Big|_{s=j\omega} = \frac{1}{1 + (j\omega)^2 LC} = \frac{1}{1 - \omega^2 LC} \tag{9}$$

The magnitude response is given by the absolute value of $H(\omega)$

$$A_v = |H(\omega)| = \left| \frac{1}{1 - \omega^2 LC} \right| = \frac{1}{\sqrt{1 + (\omega^2 LC)^2}} = \frac{1}{\sqrt{1 + \left(\frac{\omega L}{\frac{1}{\omega C}}\right)^2}} = \frac{1}{\sqrt{1 + \left(\frac{Z_L}{Z_C}\right)^2}} \quad (10)$$

Solving (10) for L

$$\begin{aligned} A_v \sqrt{1 + \left(\frac{\omega L}{\frac{1}{\omega C}}\right)^2} &= 1 \\ \sqrt{1 + \left(\frac{\omega L}{\frac{1}{\omega C}}\right)^2} &= \frac{1}{A_v} \\ 1 + \left(\frac{\omega L}{\frac{1}{\omega C}}\right)^2 &= \left(\frac{1}{A_v}\right)^2 \\ \left(\frac{\omega L}{\frac{1}{\omega C}}\right)^2 &= \left(\frac{1}{A_v}\right)^2 - 1 \\ \frac{\omega L}{\frac{1}{\omega C}} &= \sqrt{\left(\frac{1}{A_v}\right)^2 - 1} \\ \omega L &= \frac{1}{\omega C} \sqrt{\left(\frac{1}{A_v}\right)^2 - 1} \end{aligned} \quad (11)$$

So

$$L = \frac{1}{\omega^2 C} \sqrt{\left(\frac{1}{A_v}\right)^2 - 1} \quad (12)$$

For $f = 100$ Hz, $A_v = 0.1$ and $C = 100 \mu\text{F}$

$$L = \frac{1}{2\pi \cdot (100)^2 \cdot (100 \times 10^{-6})} \sqrt{\left(\frac{1}{0.1}\right)^2 - 1} \approx 2.52 \text{ H} \quad (13)$$

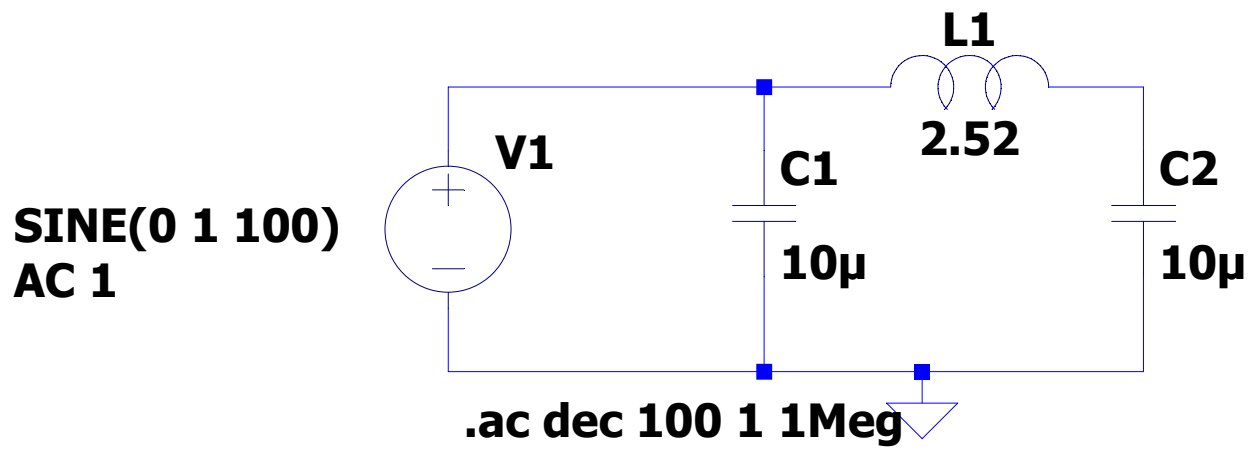


Figure 3:

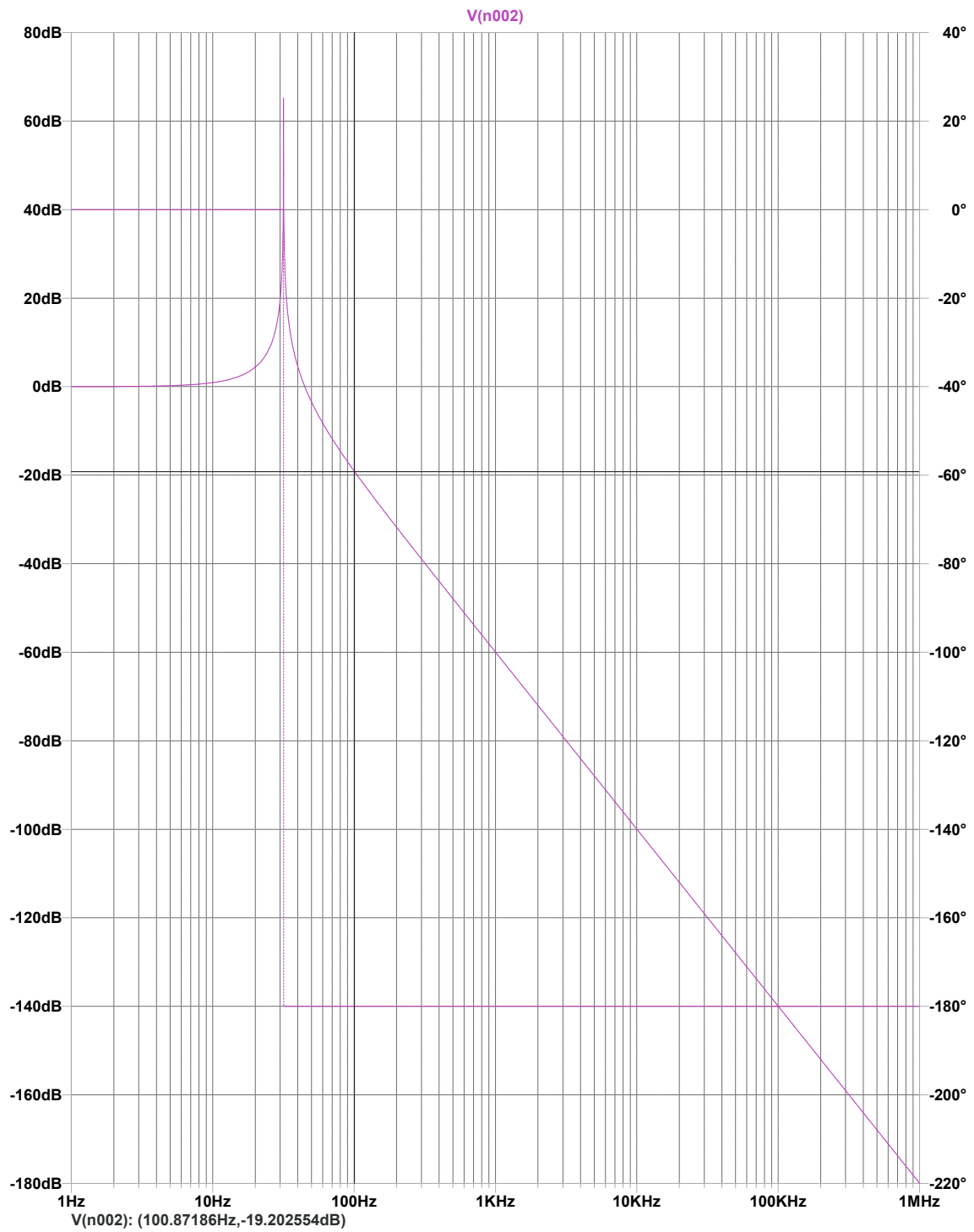


Figure 4:

As we can see in the graph on bottom left side, the V(n002) probe shows that at 100 Hz the gain in dB is ($-19.2 \approx -20dB$)

Remember that the Gain in dB is given by

$$G_{dB} = 20 \log_{10} A_v \quad (14)$$

Solving for A_v

$$A_v = 10^{\frac{G_{dB}}{20}} = 10^{\frac{-20dB}{20}} = 0.1 \quad (15)$$